



**Bangladesh University of Engineering and Technology**

**Department of Computer Science and Engineering**

Academic Year 2020 - 2021

**CSE 206**  
**Digital Logic Design Sessional**  
**Offline 2**

**Group No 2**

**Submitted by:**

1805006 - Tanjeem Azwad Zaman

1805007 - Mehbubul Hasan Al-Quvi

1805008 - Abdur Rafi

1805009 - Md. Zarzees Uddin Shah

1805010 - Anwarul Bashir Shuaib

**Date of Submission:**

April 03, 2021

# PROBLEM 1

## 1.1 PROBLEM SPECIFICATION

Design using basic gates, a 2-bit comparator to compare 2-bit numbers  $X$  and  $Y$ . The circuit should provide 3 output lines to indicate  $X > Y$ ,  $X = Y$ , and  $X < Y$ .

## 1.2 REQUIRED INSTRUMENTS

1. IC-7404 (Quantity: 1)
2. IC-7408 (Quantity: 2)
3. IC-7432 (Quantity: 1)
4. IC-7486 (Quantity: 1)
5. Input Pins (Quantity: 4)
6. Output Pin (Quantity: 3)
7. Wires
8. Software : Logisim

## 1.3 TRUTH TABLE

$A_1$	$A_0$	$B_1$	$B_0$	$G$	$L$	$E$
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	0	1	0	0	1
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	0	1	1	0	1	0
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	0	1

## 1.4 BOOLEAN EXPRESSIONS

$$\begin{aligned}
L(A_1, A_0, B_1, B_0) &= A'_1 A'_0 B'_1 B_0 + A'_1 A'_0 B_1 B'_0 + A'_1 A'_0 B_1 B_0 + A'_1 A_0 B_1 B'_0 + A'_1 A_0 B_1 B_0 + A_1 A'_0 B_1 B_0 \\
&= A'_1 B_1 (A'_0 B'_0 + A'_0 B_0 + A_0 B'_0 + A_0 B_0) + A'_1 B'_1 A'_0 B_0 + A_1 B_1 A'_0 B_0 \\
&= A'_1 B_1 (A'_0 (B'_0 + B_0) + A_0 (B_0 + B'_0)) + A'_1 B'_1 A'_0 B_0 + A_1 B_1 A'_0 B_0 \\
&= A'_1 B_1 ((B'_0 + B_0)(A'_0 + A_0)) + (A'_1 B'_1 + A_1 B_1) A'_0 B_0 \\
&= A'_1 B_1 + \overline{(A_1 \oplus B_1)} A'_0 B_0 \quad [Since, A + A' = 1; AB + A'B' = \overline{(A \oplus B)}]
\end{aligned}$$

$$\begin{aligned}
G(A_1, A_0, B_1, B_0) &= A'_1 A_0 B'_1 B'_0 + A_1 A'_0 B'_1 B'_0 + A_1 A'_0 B'_1 B_0 + A_1 A_0 B'_1 B'_0 + A_1 A_0 B'_1 B_0 + A_1 A_0 B'_1 B_0 \\
&= A_1 B'_1 (A'_0 B'_0 + A'_0 B_0 + A_0 B'_0 + A_0 B_0) + A'_1 B'_1 A_0 B'_0 + A_1 B_1 A_0 B'_0 \\
&= A_1 B'_1 (A'_0 (B'_0 + B_0) + A_0 (B_0 + B'_0)) + A'_1 B'_1 A_0 B'_0 + A_1 B_1 A_0 B'_0 \\
&= A_1 B'_1 ((B'_0 + B_0)(A'_0 + A_0)) + (A'_1 B'_1 + A_1 B_1) A_0 B'_0 \\
&= A_1 B'_1 + \overline{(A_1 \oplus B_1)} A_0 B'_0 \quad [Since, A + A' = 1; AB + A'B' = \overline{(A \oplus B)}]
\end{aligned}$$

$$\begin{aligned}
E(A_1, A_0, B_1, B_0) &= A_1 A_0 B_1 B_0 + A_1 A_0 B'_1 B'_0 + A'_1 A'_0 B'_1 B'_0 + A'_1 A'_0 B_1 B_0 \\
&= A_1 B_1 (A_0 B_0 + A'_0 B'_0) + A'_1 B'_1 (A_0 B_0 + A'_0 B'_0) \\
&= (A_1 B_1 + A'_1 B'_1) (A_0 B_0 + A'_0 B'_0) \\
&= \overline{(A_0 \oplus B_0)} \overline{(A_1 \oplus B_1)}
\end{aligned}$$

## 1.5 CIRCUIT DIAGRAM

 


Figure 1: Circuit diagram for problem 1

## PROBLEM 2

### 2.1 PROBLEM SPECIFICATION

Design a 1-bit full subtractor circuit using basic logic gates. Inputs are P, Q and R denoting minuend, subtrahend and previous borrow respectively. The outputs are D and B representing the difference and output borrow.

### 2.2 REQUIRED INSTRUMENTS

1. IC-7404 (Quantity: 1)
2. IC-7408 (Quantity: 1)
3. IC-7432 (Quantity: 1)
4. IC-7486 (Quantity: 1)
5. Input Pins (Quantity: 3)
6. Output Pin (Quantity: 2)
7. Wires
8. Software: Logisim

### 2.3 TRUTH TABLE

P	Q	R	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

### 2.4 BOOLEAN EXPRESSION (WITH SIMPLIFICATION)

$$\begin{aligned} D &= P'Q'R + P'QR' + PQ'R' + PQR \\ &= P'(Q'R + QR') + P(Q'R' + QR) \\ &= P'(Q'R + QR') + P(Q'R' + QR) \\ &= \overline{P}(Q \oplus R) + P(\overline{Q \oplus R}) \\ &= P \oplus Q \oplus R \end{aligned}$$

$$\begin{aligned}
 B &= P'Q'R + P'QR' + P'QR + PQR \\
 &= P'R(Q + Q') + P'Q(R + R') + QR(P + P') \\
 &= P'R + P'Q + QR
 \end{aligned}$$

## 2.5 CIRCUIT DIAGRAM

 


Figure 2: Circuit diagram for problem 2